

**Department of Higher Education
University of Computer Studies, Yangon
First Year (B.C.Sc./B.C.Tech.)
Final Examination
Digital Logic Fundamentals I (CST-101)
September, 2018**

Answer *all* questions.

Time allowed: 3 hours

- 1 Answer **ALL** questions. (20 marks)
- a) A pulse in a certain waveform has a frequency of 50 Hz. It repeats itself every
 - (i) 1 ms
 - (ii) 20 ms
 - (iii) 50 ms
 - (iv) 100 ms
 - b) The time interval between the 50% points on the rising and falling edges is
 - (i) rise time
 - (ii) fall time
 - (iii) pulse width
 - (iv) period
 - c) In the 2's complement form, the binary number 10010011 is equal to the decimal number
 - (i) -19
 - (ii) +109
 - (iii) +91
 - (iv) -109
 - d) The binary number 10001101010001101111 can be written in hexadecimal as
 - (i) AD467₁₆
 - (ii) 8C46F₁₆
 - (iii) 8D46F₁₆
 - (iv) AE46F₁₆
 - e) Once you measure the period of a pulse waveform, the frequency is found by
 - (i) using another setting
 - (ii) measuring the duty cycle
 - (iii) finding the reciprocal of the period
 - (iv) using another type of instrument
 - f) The Boolean expression $A + B + C$ is
 - (i) a sum term
 - (ii) a literal term
 - (iii) an inverse term
 - (iv) a product term
 - g) The domain of the expression $\overline{A}BCD + A\overline{B} + \overline{C}D + B$ is
 - (i) A and D
 - (ii) B only
 - (iii) A, B, C, and D
 - (iv) none of these
 - h) The Boolean expression $X = (A + B)(C + D)$ represents
 - (i) two ORs ANDed together
 - (ii) two ANDs ORed together
 - (iii) A 4-input AND gate
 - (iv) a 4-input OR gate
 - i) The output expression for an AND-OR circuit having one AND gate with inputs A, B and C and one AND gate with inputs D, E and F is
 - (i) $\overline{A} + \overline{B} + \overline{C} + \overline{D} + \overline{E} + \overline{F}$
 - (ii) $(\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F})$
 - (iii) $ABC + DEF$
 - (iv) $(A + B + C)(D + E + F)$
 - j) A full-adder is characterized by
 - (i) two inputs and two outputs
 - (ii) three inputs and two outputs
 - (iii) two inputs and three outputs
 - (iv) two inputs and one output

- 2 (a) A portion of a periodic digital waveform is shown in Figure 2(a). The measurements are in milliseconds. Determine (i) period (ii) frequency (iii) duty cycle (10 marks)



Figure 2(a)

- (b) (i) Subtract 173_{16} from BCD_{16} .
 (ii) Determine the decimal value of the sign-magnitude number 01110111.
 (iii) Add the BCD numbers: $01001000 + 00110100$. (10 marks)
- 3 (a) (i) Describe the functional difference between a NOR gate and a negative-AND gate. Do they both have the same truth table?
 (ii) Write the output expression for a 3-input NOR with input variables A, B, and C. (9 marks)

- (b) (i) Determine the total number of possible input combinations for a 4-input AND gate.
(ii) The waveforms in Figure 3(b) are applied to points A and B of a 2-input AND gate followed by an inverter. Draw the output waveform.

 


Fig. 3(b)

 


Fig. 4(b)

- 4 (a) (i) Develop a truth table for standard POS expression: $(A + \bar{B} + C)(A + B + \bar{C})(\bar{A} + \bar{B} + \bar{C})$ (ii) Convert the standard POS expression in (i) to an equivalent SOP expression. (iii) Use Karnaugh map to simplify the standard SOP expression in (ii). (10 marks)

- (b) Write the Boolean expression for the logic circuits in Figure 4(b). (5 marks)

- 5 (a) Implement the expression $X = \overline{(\bar{A} + \bar{B} + \bar{C})}DE$ by using NAND logic.

(9 marks)

- (b) Simplify the circuit in Figure 5(b) as much as possible.

(6 marks)

 


Fig. 5(b)

- 6 (a) (i) A 3-line-to-8-line decoder can be used for octal-to-decimal decoding. When a binary 101 is on the inputs, which output line is activated? (ii) Show the decoding logic for 000101 codes if an active-HIGH (1) output is required. (6 marks)

- (b) BCD numbers are applied sequentially to the BCD-to-decimal decoder in Figure 6(b). Draw a timing diagram, showing each output in the proper relationship with the others and with the inputs.

(9 marks)

 


Fig. 6(b)

***** END *****